

Chapter 4 Review 1

Yuanqing Miao

https://github.com/myuanqing/COMPEN331_Spring2025


In this exercise we examine in detail how an instruction is executed in a single-cycle datapath. Problems in this exercise refer to a clock cycle in which the processor fetches the following instruction word:

101011000110001000000000000010100

Assume that data memory is all zeros and that the processor's registers have the following values at the beginning of the cycle in which the above instruction word is fetched:

| r0 | r1 | r2 | r3 | r4 | r5 | r6 | r8 | r12 | r31 |
|----|----|----|----|----|----|----|----|-----|-----|
| 0 | -1 | 2 | -3 | -4 | 10 | 6 | 8 | 2 | -16 |

 - a. What are the outputs of the sign-extend and the "Shift left 2" unit (The simple control and datapath are extended to handle the jump instruction)) for this instruction word?



op field always in bits **31-26**

for lw and sw **rs** is the base

```
101011 00011 00010 0000000000010100
```

Step 1: Identify the Instruction Type

Breaking it into fields based on the MIPS instruction format:

- Opcode (bits 31-26): `101011` → This corresponds to **SW** (Store Word)
- rs (bits 25-21): `00011` → Register `$r3`
- rt (bits 20-16): `00010` → Register `$r2`
- Immediate (bits 15-0): `0000000000010100` → This is the offset.

Step 2: Sign Extend

The immediate field is `0000000000010100` (16-bit).

- This is `0x14` in hexadecimal, or **20 in decimal**.
- Since the most significant bit (MSB) is `0`, it is already non-negative.
- When sign-extended to 32 bits, it remains `00000000 00000000 00000000 00010100` (decimal 20).

Thus, **Sign-extend output:** `00000000 00000000 00000000 00010100` (decimal 20).

Step 3: Shift Left 2

The Shift Left 2 unit shifts the sign-extended immediate left by 2 bits.


- `00000000 00000000 00000000 00010100` (decimal 20)
- Shifting left by 2 bits (`<< 2`):
 - `00000000 00000000 00000000 01010000` (decimal 80)

Thus, **Shift Left 2 output:** `00000000 00000000 00000000 01010000` (decimal 80).

Final Answer:

- **Sign-extend output:** `00000000 00000000 00000000 00010100` (decimal 20).
- **Shift Left 2 output:** `00000000 00000000 00000000 01010000` (decimal 80).

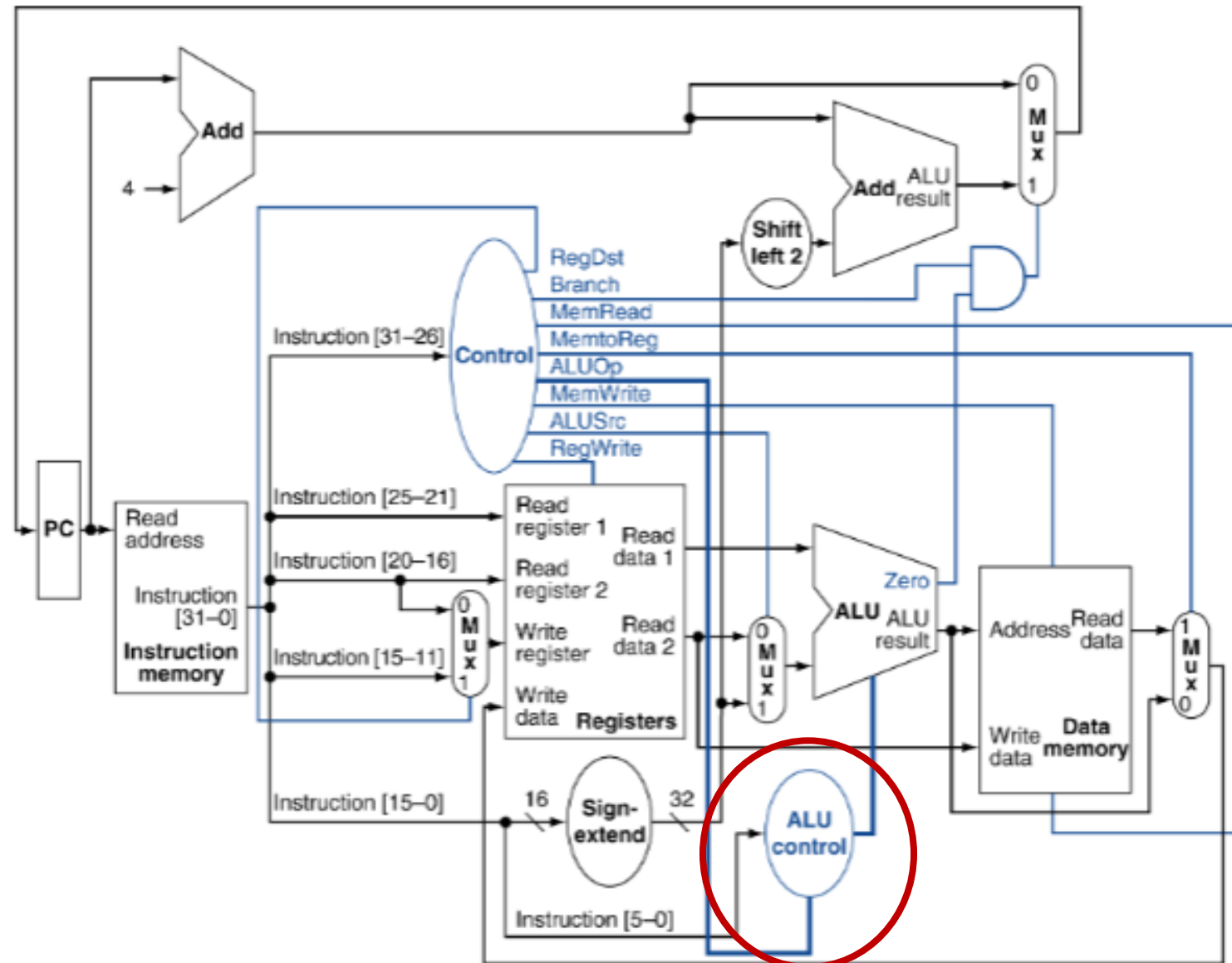b. What are the values of the ALU control unit's inputs for this instruction?



101011 00011 00010 0000000000010100


SW \$r2, 20(\$r3)

- Assume 2-bit ALUOp derived from opcode
 - Combinational logic derives ALU control

| opcode | ALUOp | Operation | funct | ALU function | ALU control |
|--------|-------|------------------|--------|------------------|-------------|
| lw | 00 | load word | XXXXXX | add | 0010 |
| sw | 00 | store word | XXXXXX | add | 0010 |
| beq | 01 | branch equal | XXXXXX | subtract | 0110 |
| R-type | 10 | add | 100000 | add | 0010 |
| | | subtract | 100010 | subtract | 0110 |
| | | AND | 100100 | AND | 0000 |
| | | OR | 100101 | OR | 0001 |
| | | set-on-less-than | 101010 | set-on-less-than | 0111 |


- ALUOp[1-0]: 00
- Instruction[5-0]: 010100 (not used for I-type instructions like SW)
- ALU Control Output: 0010 (Addition)

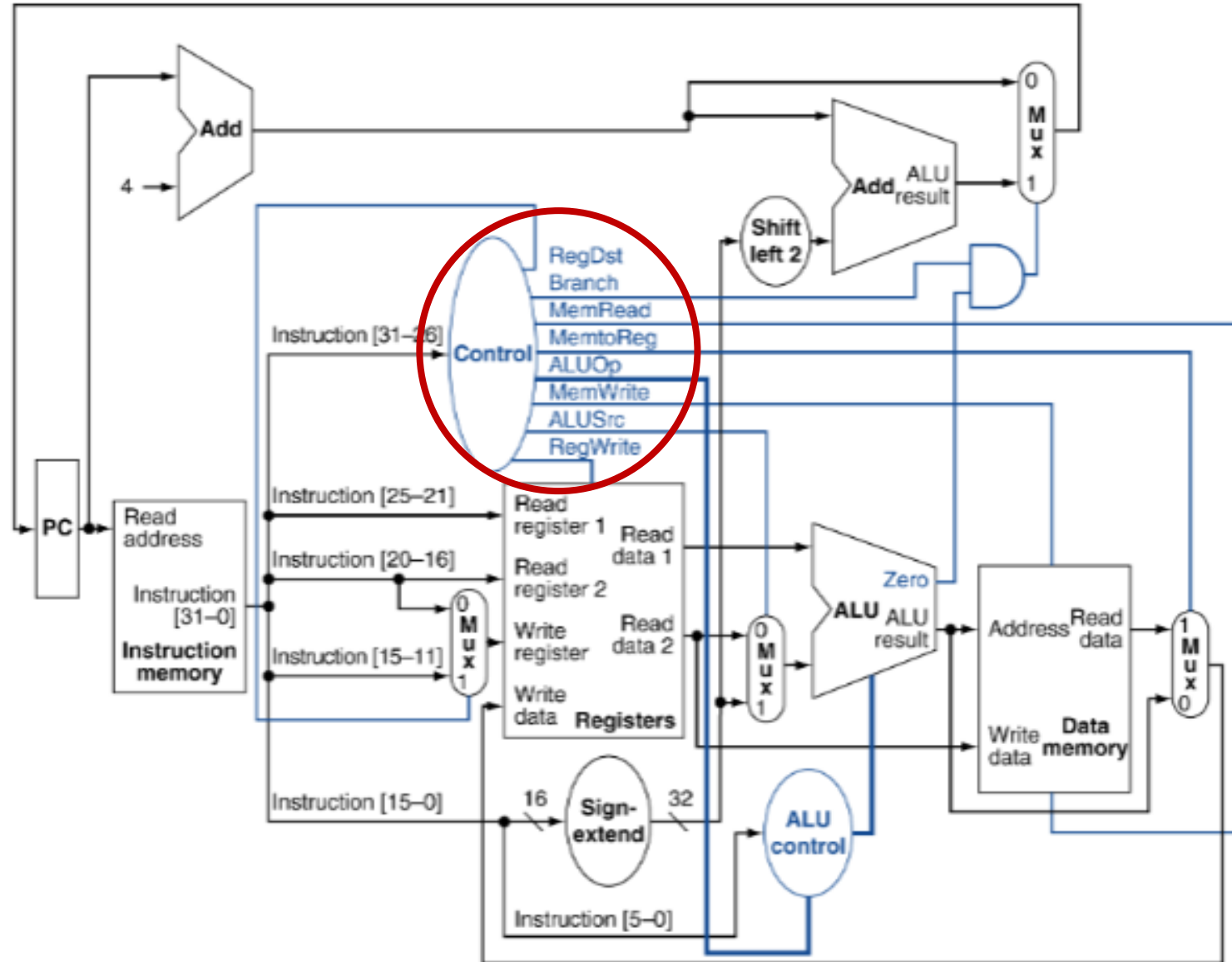c. Show the values of the control lines shown in the table.



| Control Signal | Value for <code>SW</code> | Explanation |
|----------------|---------------------------|---|
| RegDst | X (Don't care) | <code>SW</code> does not write to a register, so destination selection is irrelevant. |
| Branch | 0 | <code>SW</code> is not a branch instruction, so no branching occurs. |
| MemRead | 0 | <code>SW</code> does not read from memory; it only writes data to memory. |
| MemtoReg | X (Don't care) | No register write occurs, so the source of register data is irrelevant. |
| ALUOp | 00 | The ALU performs addition (<code>rs + offset</code>) to calculate the memory address. |
| MemWrite | 1 | <code>SW</code> writes data to memory , so memory write is enabled. |
| ALUSrc | 1 | The second ALU operand comes from the sign-extended immediate (offset) , not a register. |
| RegWrite | 0 | <code>SW</code> does not write to a register, so register write is disabled. |

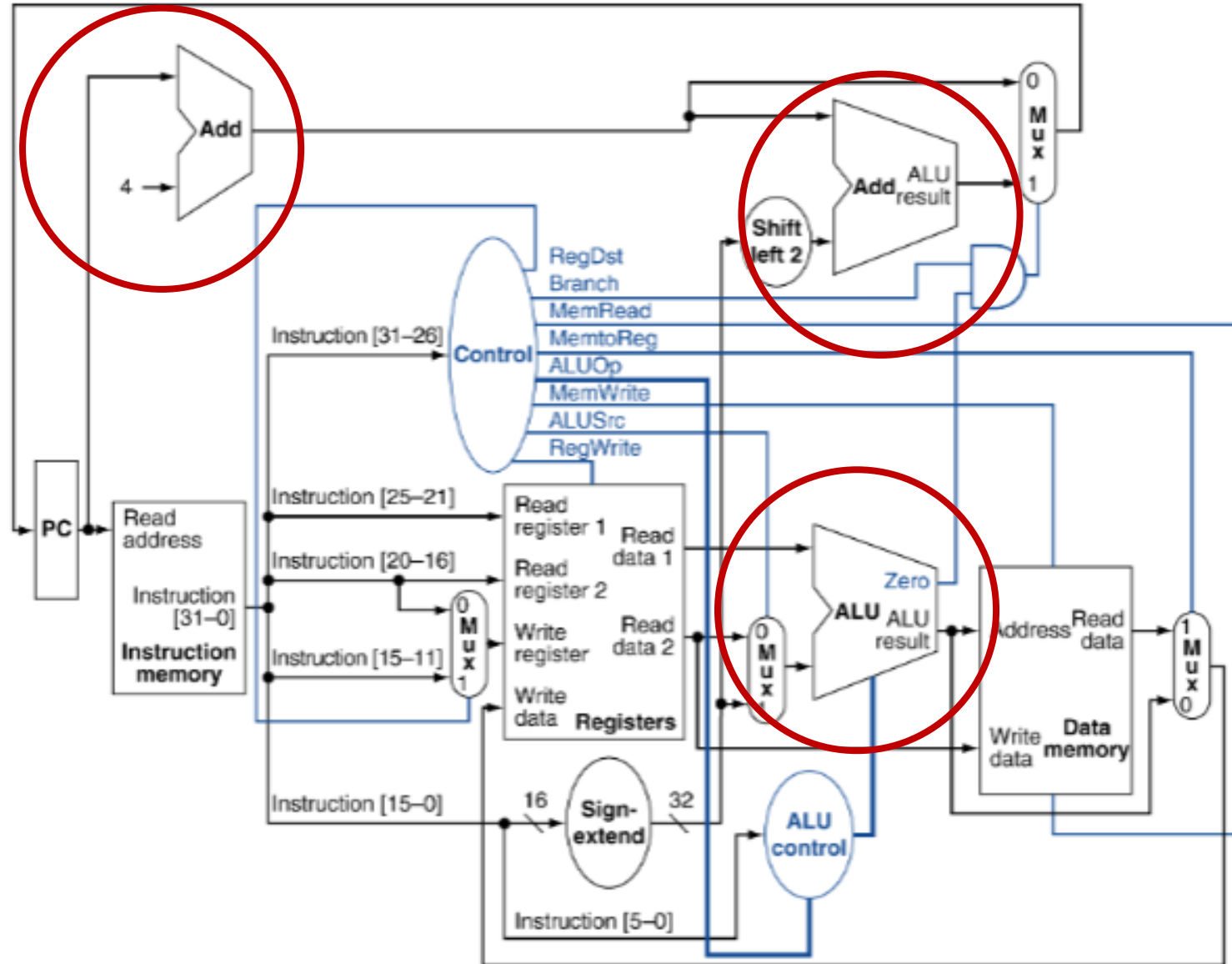d. For the ALU and the two add units, what are their data input values?



SW \$r2, 20(\$r3)

| r0 | r1 | r2 | r3 | r4 | r5 | r6 | r8 | r12 | r31 |
|----|----|----|----|----|----|----|----|-----|-----|
| 0 | -1 | 2 | -3 | -4 | 10 | 6 | 8 | 2 | -16 |

1. ALU Inputs:

- First Operand: `rs` (`$r3` = `-3`)
- Second Operand: Sign-extended immediate (`20`)
- ALU Operation: Addition (`-3 + 20 = 17`)

2. First Adder (PC + 4):

- Inputs: `PC` and `4`
- Output: `PC + 4` (new instruction address)

3. Second Adder (Branch Target Calculation):

- Inputs: Sign-Extended Immediate (shifted left 2) and `PC + 4`
- Output: Used only for branches (not applicable here)

e. What are all inputs for the "Registers" unit?



a. Registers

The **Registers Unit** has the following inputs:

- Read Register 1 (**rs**): \$r3 (value = -3)
- Read Register 2 (**rt**): \$r2 (value = 2)
- Write Register: Not used in **SW**
- Write Data: Not used in **SW**
- RegWrite: 0 (disabled)